

Clap controlled LED switching PCB design


Circuit Design:

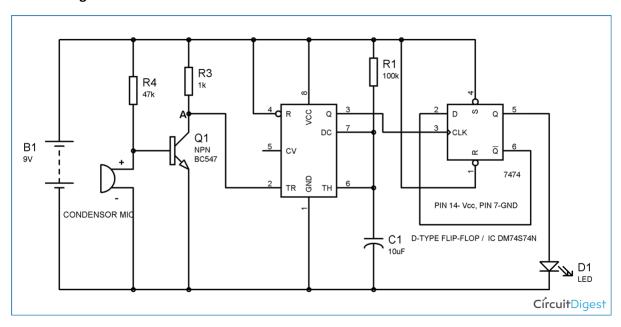


PCB layout design on ExpressPCB:

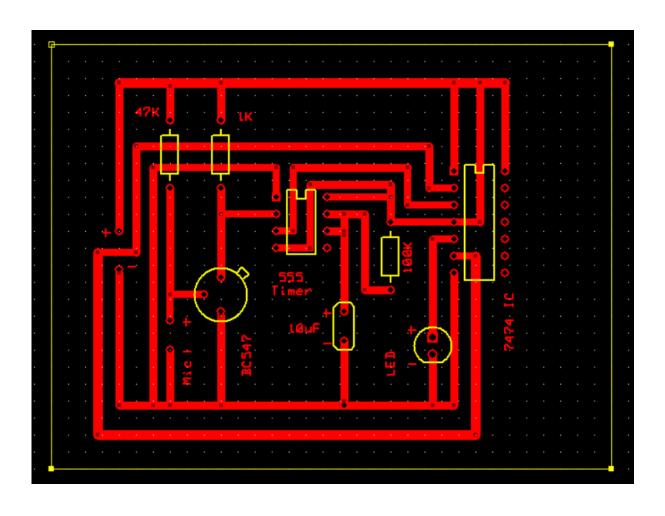

Extracted PCB layout:

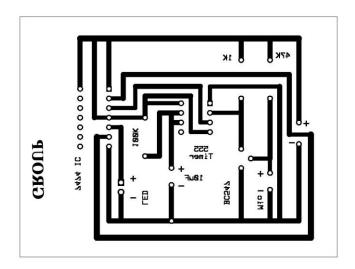

Tracing Layout on copper board:

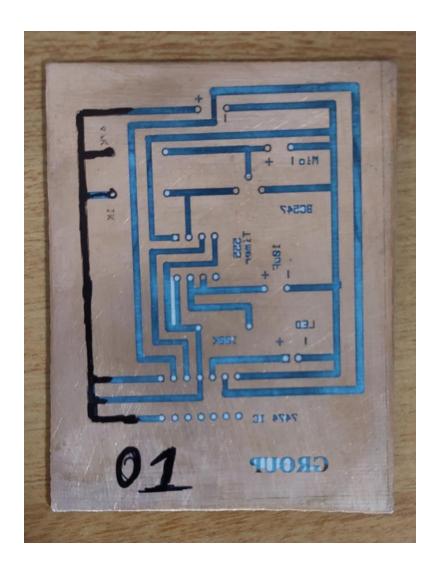

Final Circuit:

